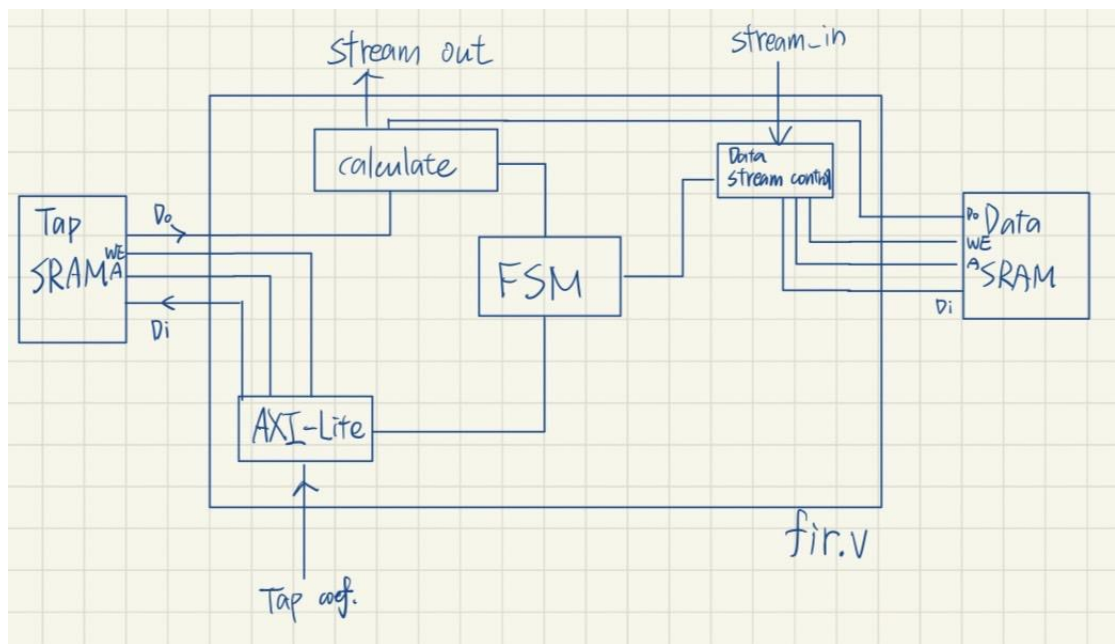


NYCU 電子研究所 呂紹愷 311510187 Lab3

● Block Diagram

電路會先讀取 tap coef.，而在這次 design 中我一次就先讀完，並都存入 TapRAM，同時我也先把 data 也一次讀取 11 個值，並放入 dataRAM，接著 tb 會先檢查我們的 coef. 是否正確，正確才會繼續跑。利用 FSM 去控制在前 11 次的乘加(因為前 11 次不會乘完全部的 coef.，因此我分成前 11 次和後面的乘加)，前 11 次乘加完就先輸出了，然後跳至 11 次後面的乘加，並要特別注意 dataRAM 和 TapRAM 的是怎麼 shift 的，在後面的報告中有更詳細的描述，控制好 data 和 tap 就可以完成此次的 FIR design 了。



● Describe operation

◆ How to receive data-in and tap parameters and place into SRAM

I. data-in

data 是透過 AXI-stream 來做傳輸，當我們把 ss_tready 拉起來，代表我們可以收 data 了，這時候 tb 就會吐值到 design。在這個 lab 中，我先把 11 個 data 放進 data SRAM，同時也把 11 個 tap 值也放進 SRAM，到計算的 state 再開始做運算，值都成完時再把舊的 data 洗掉，重新再拉 ss_tready 跟 tb 要值。

II. tap parameters


tap parameters 是透過 AXI-Lite 來做傳輸，主要要熟悉 AXI-lite 的 protocol，tb 會先傳送 data 的地址，我們要拉 awready high，這樣才知道現在傳的 data address，接著 tb 會把 wready 拉 high，代表 tb 方準備好可以寫入了，而我們的 design 準備好時再把 wvalid 拉 high，tb 就會吐值了。在這個 lab 中我也是先把 11 個值都先讀進 SRAM 存好，後

面到運算的 state 時再開始運算。

 
III. SRAM

SRAM 的操作就簡單許多，要注意的地方就三點，1. data 的地址 2. write enable 3. 輸入 data，把這三樣東西準備好，並對齊，就可以在正確的時間地點輸入進 SRAM。


◆ How to access shiftram and tapRAM to do computation



 上圖為 DataRAM 和 TapRAM 的示意圖，會去控制 `ptr`，來決定這次要從 SRAM 讀哪個位置，並讓 `ptr` 從 `initial_ptr` 跑到 `X_count` 來完成一次輸出運算。



 我分為前 11 次運算以及 12~600 次運算為一組，在前 11 次不會乘滿整個 tap，上圖為第 1 筆以及第 2 筆的運作方式，以此類推至第 11 筆。11 筆後就是全乘了，而且會需要寫新值進去 dataRAM，`initial_ptr` 也會改變，如下圖所示，藉由控制 `ptr` 來做讀取和寫，如下方波形圖所示，將 tap, data 的要乘的位置對好，再做運算。



◆ How ap_done is generated

使用計數器來看現在是第幾筆 data 輸入。

```
always @(posedge axis_clk or negedge axis_rst_n) begin
    if(~axis_rst_n)
        ap_done <= 0;
    else if(pattern_number == 600)
        ap_done <= 1;
    else
        ap_done <= ap_done;
end
```

◆ How ap_start is generated

當 awaddr==0 和 wdata==1 時就拉起來，為了讓它 hold 一個 cycle 就好，所以使用 state 來控制。

```

always @(posedge axis_clk or negedge axis_rst_n) begin
    if(~axis_rst_n)
        ap_start <= 0;
    else if(awaddr == 0 && wdata == 1 && cs != input_1 )
        ap_start <= 0;
    else if(awaddr == 0 && wdata == 1 && cs == input_1 )
        ap_start <= 1;
    else
        ap_start <= ap_start;
end

```

◆ How ap_start is generated

idle 的控制相對簡單，只需要跟 start, done 做好搭配即可。

```

always @(posedge axis_clk or negedge axis_rst_n) begin
    if(~axis_rst_n)
        ap_idle <= 1;
    else if(ap_start)
        ap_idle <= 0;
    else if(ap_done)
        ap_idle <= 1;
    else
        ap_idle <= ap_idle ;
end

```

● Resource usage

Site Type	Used	Fixed	Prohibited	Available	Util%
Slice LUTs*	314	0	0	53200	0.59
LUT as Logic	314	0	0	53200	0.59
LUT as Memory	0	0	0	17400	0.00
Slice Registers	233	0	0	106400	0.22
Register as Flip Flop	230	0	0	106400	0.22

● Timing Report

Tcl Console Messages Log Reports Design Runs Timing x			
Design Timing Summary			
<div> General Information Timer Settings Design Timing Summary Clock Summary (1) Methodology Summary > Check Timing (432) > Intra-Clock Paths Inter-Clock Paths Other Path Groups </div>			
Setup	Hold	Pulse Width	
Worst Negative Slack (WNS): 1.835 ns	Worst Hold Slack (WHS): 0.135 ns	Worst Pulse Width Slack (WPWS): 5.500 ns	
Total Negative Slack (TNS): 0.000 ns	Total Hold Slack (THS): 0.000 ns	Total Pulse Width Negative Slack (TPWS): 0.000 ns	
Number of Failing Endpoints: 0	Number of Failing Endpoints: 0	Number of Failing Endpoints: 0	
Total Number of Endpoints: 323	Total Number of Endpoints: 323	Total Number of Endpoints: 231	
All user specified timing constraints are met.			
Timing Summary - timing_1 x Timing Summary - timing_2 x Timing Summary - timing_3 x			

longest path


Max Delay Paths	
Slack (MET) : 1.835ns (required time - arrival time)	
Source:	genblk1.cs_reg[1]/C (rising edge-triggered cell FDCE clocked by axis_clk {rise@0.000ns fall@6.000ns period=12.000ns})
Destination:	genblk1.multi_result_reg[29]/D (rising edge-triggered cell FDCE clocked by axis_clk {rise@0.000ns fall@6.000ns period=12.000ns})
Path Group:	axis_clk
Path Type:	Setup (Max at Slow Process Corner)
Requirement:	12.000ns (axis_clk rise@12.000ns - axis_clk rise@0.000ns)
Data Path Delay:	10.060ns (logic 7.555ns (75.096%) route 2.505ns (24.904%))
Logic Levels:	8 (CARRY4=4 DSP48E1=2 LUT5=1 LUT6=1)
Clock Path Skew:	-0.145ns (DCD - SCD + CPR)
Destination Clock Delay (DCD):	2.128ns = (14.128 - 12.000)
Source Clock Delay (SCD):	2.456ns
Clock Pessimism Removal (CPR):	0.184ns
Clock Uncertainty:	0.035ns ((TSJ^2 + TIJ^2)^1/2 + DJ) / 2 + PE
Total System Jitter (TSJ):	0.071ns
Total Input Jitter (TIJ):	0.000ns
Discrete Jitter (DJ):	0.000ns
Phase Error (PE):	0.000ns

Slack (MET) : 1.841ns (required time - arrival time)	
Source:	genblk1.cs_reg[1]/C (rising edge-triggered cell FDCE clocked by axis_clk {rise@0.000ns fall@6.000ns period=12.000ns})
Destination:	genblk1.multi_result_reg[31]/D (rising edge-triggered cell FDCE clocked by axis_clk {rise@0.000ns fall@6.000ns period=12.000ns})
Path Group:	axis_clk
Path Type:	Setup (Max at Slow Process Corner)
Requirement:	12.000ns (axis_clk rise@12.000ns - axis_clk rise@0.000ns)
Data Path Delay:	10.054ns (logic 7.549ns (75.081%) route 2.505ns (24.919%))
Logic Levels:	8 (CARRY4=4 DSP48E1=2 LUT5=1 LUT6=1)
Clock Path Skew:	-0.145ns (DCD - SCD + CPR)
Destination Clock Delay (DCD):	2.128ns = (14.128 - 12.000)
Source Clock Delay (SCD):	2.456ns
Clock Pessimism Removal (CPR):	0.184ns
Clock Uncertainty:	0.035ns ((TSJ^2 + TIJ^2)^1/2 + DJ) / 2 + PE
Total System Jitter (TSJ):	0.071ns
Total Input Jitter (TIJ):	0.000ns
Discrete Jitter (DJ):	0.000ns
Phase Error (PE):	0.000ns

- Simulation Waveform

- ◆ Coefficient program, and read back

 先把 11 個 coef.寫進 TapRAM，tb 要檢查時則透過 AXI-lite 去做資料傳輸。




- ◆ Data-in stream-in

前 11 筆 data 直接拿，後面 data 則是有需要才拿




- ◆ Data-out stream-out

在 cs ==7 的時候輸出正確 data

 

- ◆ Bram access control

前 11 筆 data 直接連續存進 SRAM

 

◆ FSM

在 state1 是把要存進 tapRAM 的地址準備好，state2 時寫入 tapRAM

[illegible]

在 state 3,4 時，會做運算，把 tap 和 data 的值都對齊來做乘法，3, 4state 差別在於是否有乘滿整個 tap coef.。

\genblk1.cs[3:0]=4	3	4												
\genblk1.ns[3:0]=4	3	4	5											
\genblk1.coef_ptr[3:0]=10	9	8	7	10	9	8	7	6	5	4	3	2	1	0
\genblk1.ptr[3:0]=0	2	3	4	0	1	2	3	4	5	6	7	8	9	10

在 5, 6, 7 則是做最後一次乘法，然後累加，輸出數值，並把新 data 寫進 dataRAM。

\genblk1.cs[3:0]=4	3	4							5	6	7	4					
\genblk1.ns[3:0]=4	3	4							5	6	7	4					
\genblk1.coef_ptr[3:0]=10	9	8	7	10	9	8	7	6	5	4	3	2	1	0		10	
\genblk1.ptr[3:0]=0	2	3	4	0	1	2	3	4	5	6	7	8	9	10	0		1

```
always@(*) begin
    case(cs)
        idle: //0
            begin
                ns = input_1;
            end

        input_1: // 1
            // addr
            begin
                if(awaddr == 12'h000 && wdata == 32'd1)
                    ns = calculate_1 ;
                else if(awvalid)
                    ns = input_2;
                else
                    ns = input_1;
            end

        input_2:
            // write
            begin
                if(awaddr == 12'h000 && wdata == 32'd1)
                    ns = calculate_1;
                else if(wvalid)
                    ns = input_1;
                else
                    ns = input_2;
            end

        calculate_1 : //2
            begin
                if(out_count == 10)
                    ns = calculate_2;
                else
                    ns = calculate_1;
            end
    end
end
```

```

        calculate_2 : //3
        begin
            if(X_count == ptr )
                ns = last_multi;
            else
                ns = calculate_2;
            end

        last_multi:
        begin
            ns = accumulate;
        end

        accumulate:
        begin
            ns = out_state;
        end

        out_state :
        begin
            ns = calculate_2;
        end

        default:
            ns= idle;
        endcase
    end
end

```